

F.Y.B.Sc. (CBCS)-Regular-Semester 2017 Sem I
USELT01 - Electronics Paper-I
(Network Analysis and Digital Fundamentals)

P. Pages : 2

Time : Three Hours



GUG/W/17/10085

Max. Marks : 50


- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat diagram wherever necessary.
 3. Use of log table/calculator is permissible.

Either

1. a) Explain the ideal voltage source and current source. How does it differ from practical sources ? 4+
6
Explain the Kirchoff's current law and Kirchoff's voltage law with suitable examples.


OR

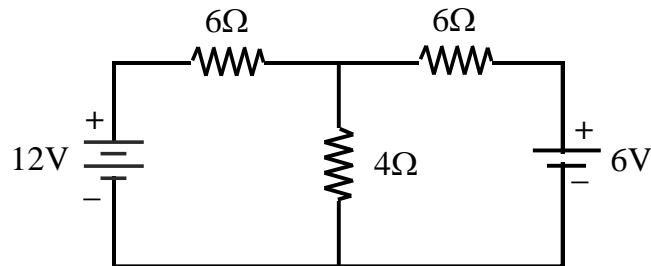- b) State and explain superposition theorem. Using Superposition theorem, calculate the current through 4Ω resistor in following circuit. 6+
4




Either

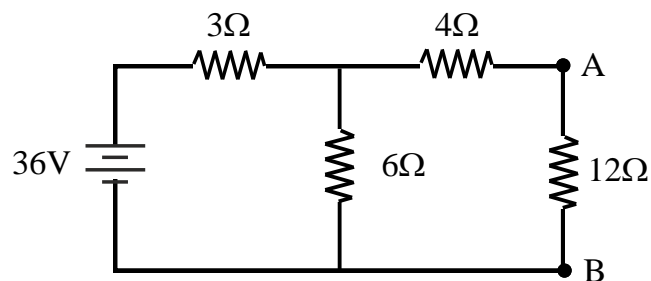2. a) State and prove Norton's theorem. Using Norton's theorem, calculate the current through the 12Ω resistor shown in following circuit. 6+
4



OR

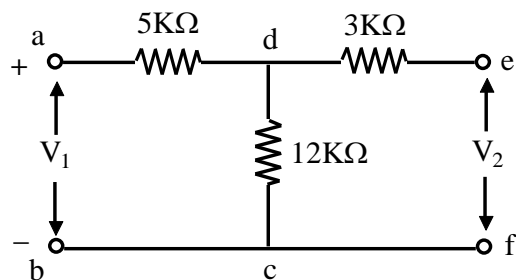- b) Explain z-parameter of two port network. Draw basic Z parameter equivalent circuit find the z-parameter for the network shown in following circuit. 6+
4



Either

3. a) What is hexadecimal number system ? Explain the conversion method of Hexadecimal to decimal number and decimal number to hexadecimal number with suitable example. 10

OR

- b) What is code ? Explain 8421 and excess-3 code with suitable examples. 2+
4+
4

Either

4. a) What is logic gate ? Explain all basic gates Explain the construction of basic gates using NAND gate. 4+
6

OR

- b) State and prove DeMorgan's theorem. Explain the 4-bit controlled inverter using XOR gate. 5+
5

5. Attempt **any ten** of the followings. 10

- a) What is Mesh analysis ?
- b) Draw diagram for star network.
- c) What is duality of network ?
- d) State Thevenins theorem.
- e) What is two port network ?
- f) State maximum power transfer theorem.
- g) What is binary number system ?
- h) What is parity code ?
- i) What is 1's complement ?
- j) Draw the symbol of NAND and NOR gate.
- k) Draw the logic diagram of XOR gate using basic gates.
- l) Draw the symbol of XNOR gate and give its truth table.
