

F.Y.B.Sc. (With Credits)-Regular-Semester 2012 Sem I
E-02-Electronics : Paper-II (Transducers and Network Theorems)

P. Pages : 2

Time : Three Hours



GUG/S/17/3308

Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw a neat and labelled diagram wherever necessary.
 3. Use of log table / calculator is allowed.

Either

1. a) What is thermistor ? Explain construction and working of thermistor. 5+5
Explain the construction and working of thermocouple.

OR

- b) Explain construction and working of LVDT. Draw its characteristics and explain. 10
State the advantages of LVDT.

Either

2. a) What is LDR ? Explain the construction and working of LDR. State any four uses of LDR. 7+3
Explain working of photovoltaic cell.

OR

- b) What is LCD ? Explain construction and working of dynamic scattering type LCD. 6+4
Explain the working of LASER diode.

Either


3. a) Explain ideal and practical voltage source with suitable diagram. 5+5
Explain ideal and practical current source with suitable diagram.

OR

- b) State and prove - 5+5
i) Kirchoff's voltage law
ii) Kirchoff's current law


Either

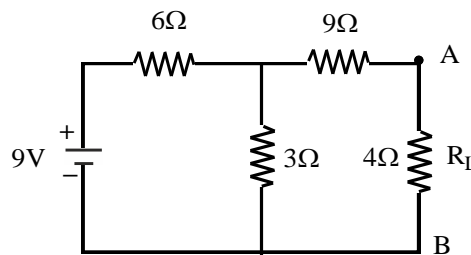4. a) State and prove Thevenin's theorem. 7+3
Using Thevenin's theorem, calculate current through R_L in the following circuit :




OR

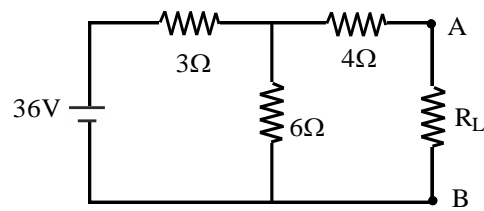- b) State and prove maximum power transfer theorem. 7+3
 In the circuit given below, find the value of load resistor R_L to be connected across Terminal A and B which would abstract maximum power from the circuit. Also find maximum power.



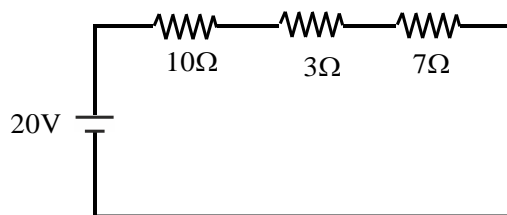5. a) Define active and passive transducers. Give two examples of each. 2½
 b) State any five uses of LED. 2½
 c) Find the voltage across each resistor using voltage divider method in the following circuit. 2½



- d) State and explain Milliman's theorem. 2½
