

B.Sc.F.Y. (With Credits)-Regular-Semester 2012 Sem I
E-02 - Electronics: Paper-II (Transducers and Network Theorems)

P. Pages : 2

Time : Three Hours



GUG/W/16/3308

Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw a neat and labelled diagram wherever necessary.
 3. Use of log table / Calculator is allowed.

1. Either

- a) Explain construction and working of microphone. Explain the working of loudspeaker with suitable diagram. **10**

OR

- b) What is piezoelectric effect? Explain construction and working piezoelectric transducer. Explain the working of unbonded type strain gauge. **10**

2. Either


- a) What is solar cell? Explain the construction and working of solar cell with suitable diagram. Draw its V-I characteristics and explain. State any four uses of solar cell. **10**

OR

- b) Explain the construction and working of LED. State its any four uses. State the materials used in construction of LED. Explain the working of photovoltaic cell. **10**

3. Either

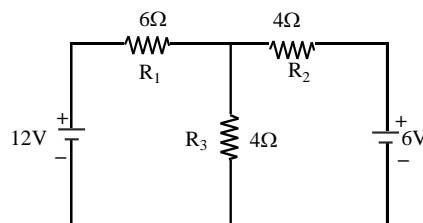- a) State and explain superposition theorem. Using superposition theorem, calculate current in resistor R_3 of the network given below:- **10**




OR

- b) Explain ideal and practical voltage source with suitable diagram. State and prove Kirchhoff's current law. **10**


4. Either

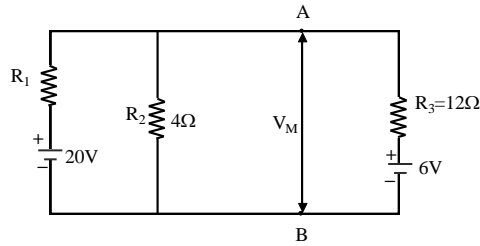- a) State and prove Milliman's theorem. Using Milliman's theorem calculate the voltage ' V_m ' across point A and B in circuit given below:- 10




OR

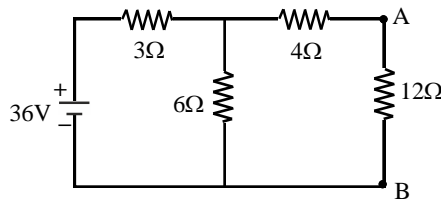- b) State and prove Norton's theorem. Using Norton's theorem find current flowing through 12Ω resistor in the following circuit. 10



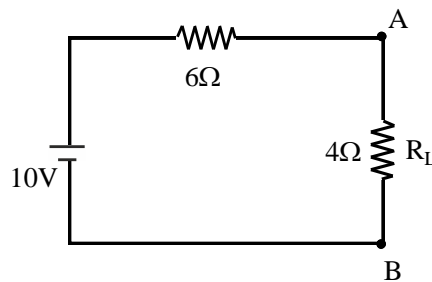5. a) What is strain gauge? Define gauge factor 'State the types of strain gauge'. 2½
- b) State any five uses of LDR. 2½
- c) Transform following voltage source into current source. 2½



- d) State and explain Thevenin's theorem. 2½
