

F.Y.B.Sc. (With Credits)-Regular-Semester 2012 Sem I
E-01 - Electronics Paper-I
(Basic Electronics and Semiconductor Devices)

P. Pages : 2

Time : Three Hours




GUG/W/17/3307

Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat diagram wherever necessary.
 3. Use of log table / calculator is permissible.

1. Either

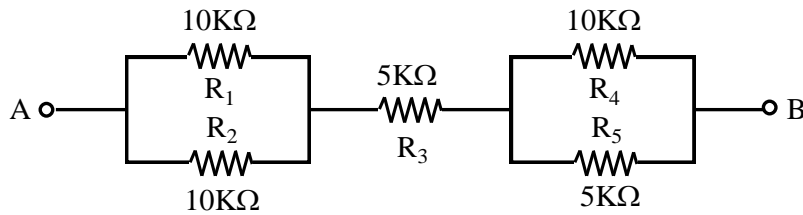- a) Explain the construction and working of potentiometer. **10**
Find the equivalent resistance across terminals A & B.



OR

- b) What is Capacitor ? Describe the basic construction of Electrolyte capacitor. **10**
Explain the construction and working of transformer.

2. Either

- a) Explain the p-type and n-type semiconductor. **10**
Draw the forward characteristics of p-n junction diode and explain it.

OR

- b) Explain the avalanche and Zener breakdown mechanism.
What is rectifier ? Explain the working of bridge full wave rectifier. Draw its input and output waveform.

3. Either

- a) Explain the construction and working of NPN transistor. **10**
Prove $\alpha = \frac{\beta}{1 + \beta}$ and $\beta = \frac{\alpha}{1 - \alpha}$

OR

- b) Explain the input and output characteristic of BJT in common emitter configuration with suitable diagram.
What is quiescent point ? Explain the importance of quiescent point.

Either

4. a) Explain the working of N-channel JFET with suitable diagram. **10**
Draw the drain characteristic of JFET and explain it.

OR

- b) Explain the construction and working of SCR.
Explain the working of TRIAC and draw its V-I characteristics.
5. a) What is step up and stepdown transformer ? **2½**
- b) Explain diode as a halfwave rectifier. **2½**
- c) Define α and β . If $\alpha = 0.95$, find β . **2½**
- d) Differentiate JFET and BJT. **2½**
