

B.Sc. I (With Credits)-Regular-Semester 2012 Sem II  
**2SELE-T2-Electronics-II : Paper-II (Measuring Devices)**

P. Pages : 1

GUG/S/16/5574

Time : Three Hours



Max. Marks : 50

- Notes :
1. All questions are compulsory.
  2. All questions carry equal marks.
  3. Draw neat and well labelled diagram wherever necessary.
  4. Use of log table calculator is allowed.

**1. Either:**

- a) How will you convert PMMC galvanometer into DC Ammeter? Explain **10**  
A 1.5 mA meter movement with an internal resistance of  $105 \Omega$  is to be converted into 0-150mA ammeter . Calculate the value of the shunt resistance required.

**OR**

- b) Explain the working of shunt type ohmmeter. **10**  
What are the merits and demerits of multimeter? Enlist the uses of multimeter.

**2. Either:**

- a) Explain with suitable diagram working of Owen's bridge and obtain the balance condition of bridge. **10**  
The impedance connected in the arms of a balanced ac bridges are as  $Z_1 = 200 + j400 \Omega$ ,  $Z_2 = 300 \Omega$ ,  $Z_3 = 150 + j100 \Omega$  calculate  $Z_4 = ?$

**OR**

- b) Explain the construction and working of EVM using FET. **10**  
State the advantages of digital multimeter.

**3. Either:**

- a) Draw the well labelled diagram of CRT and explain it. **10**

**OR**

- b) Draw the circuit diagram of relaxation oscillator using UJT and explain its working. **10**  
What is the need of delay line? Explain.

**4. Either:**

- a) Explain the use of CRO for the measurement of frequency by using Lissajous method. **10**  
A Lissajous pattern obtain on CRO has 5 horizontal tangencies and one vertical tangencies, calculate unknown frequency if known frequency is 300Hz. Draw such figure.

**OR**

- b) Draw the block diagram of dual trace CRO and explain the function of each block. **10**  
Differentiate between dual trace and dual beam CRO.

- 5. a) Explain the use of PMMC to measure dc voltage. **2½****

- b) The impedances of a.c bridge are given as follows. **2½**  
 $Z_1 = 150 \Omega \angle 60^\circ$  (inductive impedance)  
 $Z_2 = 250 \Omega$  (pure resistance)  
 $Z_3 = 400 \Omega$  (inductive impedance)  
 $Z_4 = ?$

Determine the value of  $Z_4$  arm.

- c) Explain the horizontal and vertical deflection system used in CRO in brief. **2½**

- d) Explain how will you measure as/dc voltage with CRO. **2½**

\*\*\*\*\*