



GUG/W/15/5574

B.Sc. (Part-I) (With Credits)-Regular-Semester 2012 Sem II

2SELE-T2 Electronics-II
(Measuring Devices)

Paper- II

P. Pages : 3

Time : Three Hours

Max. Marks : 50

-
- Notes :
1. All questions are compulsory.
 2. All questions carry equal marks.
 3. Draw neat and labelled diagram wherever necessary.
 4. Use of log table calculator is allowed.

1. Either

- a) Explain how will you convert PMMC **5+**
galvanometer into dc ammeter. **5**

1mA meter movement with an internal resistance of 100Ω is to be converted into 0-100mA-ammeter. Calculate the value of the shunt resistance required.

OR

- b) Explain shunt type ohmmeter with suitable diagram **5**

Explain the concept of loading effect with suitable example. **5**

2. Either

- a) Draw the diagram of AC bridge and obtain the condition of balance **5+5**

In ac bridge the impedance of arms are given as

$$Z_1 = 250\Omega \angle 180^\circ$$

$$Z_2 = 450\Omega$$

$$Z_3 = 300\Omega \angle -30^\circ$$

Determine Z_4

OR

- b) Draw the block diagram of digital multimeter and explain the function of each block. **5+5**

Explain the working of Owen's bridge and obtain the balance condition for it.

3. Either

- a) Draw the block diagram of CRO and explain function of each block state the applications of CRO. **7+3**

OR

- b) Draw the diagram of CRT and explain its working **6+4**
Explain the concept of synchronization in CRO.

4. Either

- a) Explain the use of CRO for frequency measurement using **7+3**
- i) Time base circuit.
 - ii) Lissajous Figure method.

Find the unknown frequency using Lissajous figure which has 4 vertical tangencies and 1 Horizontal tangency and frequency given to x-plate is 500Hz.

OR

- b) Draw the diagram of passive probe and explain. Explain working of dual trace CRO with block diagram. **4+6**
- 5. a)** Explain how to convert PMMC galvanometer in dc voltmeter. **2½**
- b) Draw the diagram of EVM using FET. **2½**
- c) Explain the needs of delay line. **2½**
- d) Explain use of CRO for ac voltage measurement. **2½**
