## F.Y.B.Sc. (With Credits)-Regular-Semester 2012 Sem II 2SELE-T2 - Electronics Paper-II (Measuring Devices)

	ages : e : Thi	1 ree Hours $\star 0 4 2 7 \star$	GUG/W/17/55 Max. Marks	
	Notes	<ul> <li>s: 1. All questions are compulsory and carry equal marks.</li> <li>2. Draw neat and well labelled diagram wherever necessary.</li> <li>3. Use of log table/calculator is allowed.</li> </ul>		
		EITHER		
1.	a)	What is PMMC? Explain the conversion of PMMC into DC voltmeter.	Define sensitivity	10
		OR		
	b)	<ul> <li>Explain how d' Arsonval movement will be converted to measure DC cu A 1mA meter movement with an internal resistance of 100Ω is to 10-100mA ammeter. Calculate the value of the shunt resistance required.</li> </ul>		10
		EITHER		
2.	a)	Explain the construction and working of EVM using FET. State its adva	ntages	10
	u)	OR	intergeo.	10
	b)	Obtain balance condition of ac bridge. In an a.c. bridge, find out the impedance $Z_1$ in a balanced AC bridg $Z_2 = 250\Omega$	e in which	10
		$Z_3 = 400 \Omega \angle 30^\circ$		
		$Z_4 = 100\Omega \angle -50^{\circ}$		
		EITHER		
3.	a)	Draw block diagram of CRO and explain the working of each block. Ex sensitivity in CRO.	plain deflection	10
		OR		
	b)	Explain the working of time base circuit used in CRO.Define : a) Fluorescenceb)Phosphorescence		10
		EITHER		
4.	a)	Explain passive probes used for CRO. Explain how voltage can be meas OR	sured with CRO.	5+5
	b)	Draw the block diagram of dual trace CRO and explain its working.		10
5.	a)	Explain the loading effect of voltmeter.		<b>2<sup>1</sup>/</b> <sub>2</sub>
	b)	Obtain the balance condition in schering bridge.		2 <sup>1</sup> / <sub>2</sub>
	c)	Explain the concept of synchronization in CRO.		<b>2<sup>1</sup>/</b> <sub>2</sub>
	d)	Explain how the phase can be measured with CRO.		21/2
		****		