

F.Y.B.Sc. (With Credits)-Regular-Semester 2012 Sem II
2SELE-T2-Electronics-II : Paper-II (Measuring Devices)

P. Pages : 2

Time : Three Hours



GUG/W/16/5574

Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat and well labelled diagram wherever necessary.
 3. Use of log table/calculator is allowed.

Either :

1. a) What is PMMC? **1+6+3**
Explain conversion of PMMC into series type ohmmeter.
State atleast three applications of ohmmeter.

OR


- b) Design an Ayrton shunt to provide an ammeter with current ranges 1A, 5A and 10A, if PMMC meter has internal resistance of $50\ \Omega$ and full scale current of 1mA . **10**

Either :

2. a) Draw block diagram of digital multimeter and describe in brief. **7+3**
State advantages of digital multimeter.

OR

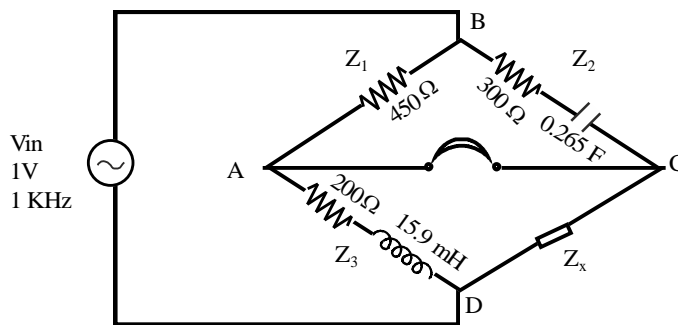- b) Obtain balance conditions of ac bridge. **5+5**
Find Z_x for the following bridge.



Either :

3. a) Draw block diagram of CRO and explain the working of each block. **7+3**
Explain deflection sensitivity in CRO.

OR

- b) Explain electrostatic focussing in CRO with suitable diagram. **10**

Either :

4. a) Explain passive probe used for CRO. **4+6**
Explain how the phase and frequency can be measured with CRO.

OR

- b) Draw block diagram of dual – trace CRO and explain. **10**
5. a) Explain the loading effect of voltmeter. **2½**
- b) Obtain the balance condition in Owen's bridge. **2½**
- c) Explain time base circuit using UJT. **2½**
- d) A lissajous pattern obtained on CRO has 5 horizontal tangencies and one vertical tangency. Calculate unknown frequency, if known frequency is 300Hz. Draw such figures. **2½**
