

B.Sc. (Part-II) (With Credits)-Regular-Semester 2012 Sem III
B.Sc.23132 - Electronics-II (Digital Electronics - I) Paper- II

P. Pages : 2

Time : Three Hours



GUG/S/16/3337

Max. Marks : 50

-
- Notes : 1. All questions are compulsory and carry equal marks.
2. Draw neat and labelled diagrams wherever necessary.
3. Use of log table and calculator are allowed.

1. Either

- a) For the given logic equation $f(A, B, C) = ABC + B\bar{C}D + \bar{A}BC$ **5**
i) Draw a truth table
ii) Simplify using k-map

For the given logic equation $f(A, B, C, D) = \pi M(0, 1, 6, 7, 8, 11, 12, 14, 15)$ **5**

- i) Write the logic equation in POS form
ii) Simplify using k-map

OR

- b) What is demultiplexer ? Explain the operation of 1:4 DEMUX. using basic gates. Design 1:8 DEMUX using 1:4 DEMUX. **6+4**

2. Either

- a) What is encoder? **2+8**
Draw the logic diagram of decimal to BCD encoder & explain its working with truth table.

OR

- b) What is half adder? Explain it with logic diagram and truth, table. **5+5**
Draw the logic diagram of 4 bit binary adder. Explain its working.

3. Either

- a) What is meant by clocked flip flop? Explain the working clocked SR FF. Also draw the timing diagram. **10**

OR

- b) What is the main disadvantage of JK FF? How is it overcome in JKMS FF? Explain. **10**
What is toggle flip flop? State its application.

4. Either

- a) What is meant by modulus of a counter? How the required number of flip flops are calculated in modified counter. Draw the logic diagram of 4 bit down counter and explain its working. Write the count sequence and draw the timing diagram. **10**

OR

- b) How many flip flops are required for mod 9 counter? Design and explain the mod-8 up synchronous counter. Write the count sequence for the counter. **2+8**

- 5.** a) What is Karnaugh map? Draw the two and four variable k-map. **2½**

- b) Explain 2 line to 4 line decoder. **2½**

- c) What is meant by: **2½**

i) Active high preset / clear inputs.

ii) Active low preset / clear inputs.

- d) A synchronous counter is faster than an asynchronous counter. Justify the statement. **2½**
