



Electronics - II (Digital Electronics - I)
Paper - II

P. Pages : 3

Time : Three Hours

Max. Marks : 50

- Notes : 1. All questions are compulsory and carry equal marks.
2. Draw neat and well labelled diagram wherever necessary.
3. Use of log table and calculator is allowed.

1. Either

- a) Draw a logic circuit for the Boolean equation: **4+**
6
 $Y = (A + BC)(B + \bar{C}A)$
Convert the above equation in SOP forms and implement it using NAND gates.

OR

- b) What is demultiplexer? **1+**
Draw the logic diagram of 1:4 DEMUX and explain its working. **4+**
5
Obtain the 1:8 DEMUX using 1:4DEMUX.
Explain its working with truth table.

2. Either

- a) Describe BCD to 7-segment decoder/driver **10**
and explain how it helps in showing
different decimal digits in the display.

OR

- b) What is full adder? **1+**
Draw logic diagram of full adder and **3+**
explain its working. **6**
Draw 4-bit 2's complement
Adder/subtractor circuit and explain its
working.

3. Either

- a) Explain the construction and working of **3+**
JKFF. State its limitations. **2+**
How is it eliminated in JKMSFF? Explain. **5**

OR

- b) What is flip-flop? Explain construction and **6+**
working of clocked RSFF. and give its truth **4**
table.
Explain the following
i) Edge and level triggering
ii) Propagation delay
iii) Set up time, and
iv) Hold time.

4. Either

- a) Explain the construction and working of asynchronous 4-bit binary-up counter. **5+**
Draw its timing diagram. Why is it called ripple counter? **1+**
The output of a ripple counter is DCBA=1001. After how many clock pulses the counter will have the same state? **4**
Explain.

OR

- b) What is ring counter? How does it differ from a normal counter? **1+**
Explain the construction and working of a 4-bit ring counter using JKMSFFs. State uses of ring counter. **2+**
5+
2
- 5.** a) What is K-map? Explain. It with 3 variables. **2.5**
- b) Draw logic diagram of half- adder. Give its truth table and Boolean equations. **2.5**
- c) What is DFF? Explain. **2.5**
- d) Draw the logic diagram of mod-8 synchronous counter and give its truth table. **2.5**
