



GUG/W/15/3337

B.Sc. (With Credits)-Regular-Semester 2012 Sem III

**B.Sc.23132 Electronics-II : Digital
Electronics -I Paper- II**

P. Pages : 4

Time : Three Hours

Max. Marks : 50

-
- Notes :
1. All questions carry equal marks and are compulsory.
 2. Draw a diagram wherever necessary.
 3. Use of log table / calculator is allowed.

1. Either :

- a) What is a multiplexer ? Explain the concept of N:1 multiplexer with suitable block diagram. **5**
- b) Construct 8:1 multiplexer using 4:1 multiplexer. Draw its truth table. **5**

OR

- c) What is k-map ? Explain k-map for 2, 3 and 4 variables with examples. **5**

- d) Plot a k-map for the expression **5**
 $f(A, B, C, D) = \sum m(0, 2, 3, 4, 8, 9, 10, 11)$
and simplify it in SOP form.

2. Either :

- a) What is decoder ? Draw logic diagram of 2-line to 4-line decoder and explain its working with truth table. **5**
- b) Explain the working of decimal to BCD encoder with its truth table and logic diagram. **5**

OR

- c) Explain the construction and working of BCD to 7-segment decoder / driver. **5**
- d) What is full adder ? Draw its logic diagram. Give its truth table and Boolean equation. **5**

3. Either :

- a) Explain the construction and working of RS flipflop using NOR gates. Give its truth table. **5**

- b) State the drawback of clocked RSFF. **5**
Explain how the drawback can be overcome using D-flipflop.

OR

- c) Explain the importance of preset and clear inputs in flip flop. What do you mean by active high and active low preset and clear ? **5**
- d) Explain construction and working of JKMS flipflop. **5**

4. Either :

- a) Explain the construction and working of 4 bit ripple counter. Give its timing diagram. **5**
- b) What is modulus of counter ? Explain its concept with suitable example. State the member of flipflops required for the construction of. **5**
- i) MOD-16
- ii) MOD-100 counter.

OR

- c) Differentiate between synchronous and asynchronous counter. **5**
- d) Explain the construction and working of 3-bit ring counter. Give its timing diagrams. **5**

5. Either :

- a) Design 1:8 Demux using 1:4 Demux. **10**
- b) Draw circuit for 4bit 2's complement adder / subtractor.
- c) Explain the working of T-FF.
- d) Explain the working of 3-bit Johnson counter with suitable timing diagrams.
