

S.Y.B.Sc. (With Credits)-Regular-Semester 2012 Sem III
B.Sc.23132-Electronics Paper-II (Digital Electronics-I)

P. Pages : 1

Time : Three Hours



GUG/W/17/3337

Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat and labelled diagrams wherever necessary.
 3. Use of log table / calculator is allowed.

1. Either

- a) Reduce the expression $f = \sum m(0, 2, 3, 4, 5, 6)$ using k-map and draw the logic circuit. 7+
Explain SOP form with suitable example. 3

OR

- b) Draw logic diagram for 4:1 multiplexer using logic gates and explain its truth table. 5+
What is demultiplexer ? Explain the operation of 1:4 DEMUX with logic diagram using logic gate. 5

2. Either

- a) Draw the logic diagram of 1 of 10 decoder using logic gates and give its truth table. 5+
What is Encoder ? Draw the block diagram of decimal to BCD encoder and give its truth table. 5

OR

- b) What is full adder ? Explain 3+
Draw the logic diagram of 2's complement adder / subtractor (4 bit). Explain its working with suitable example. 7

3. Either

- a) Explain the working of JKFF with suitable diagram. 5+
What is race around condition ? How it can be removed ? Explain. 5

OR

- b) Give the advantages of present and clear input of flip flop. 3+
Explain the working of T flip flop with suitable logic diagram. 7

4. Either

- a) Explain the working of 4-bit ripple counter with truth table and timing diagram. 7+
What is down counter ? Explain. 3

OR

- b) With the help of logic diagram and timing diagram, explain the working of 3-bit synchronous counter. 5+
Explain the working of Johnson counter with suitable logic diagram. 5

- 5.**
- a) Reduce the expression $f = \overline{A}\overline{B} + \overline{A}B + AB$. 2½
 - b) Draw the circuit diagram for common cathod type display using IC 7448. 2½
 - c) Explain the working of RS flip flop. 2½
 - d) Give the applications of counter. 2½
