

S.Y.B.Sc. - II (With Credits)-Regular-Semester 2012 Sem III
B.Sc.23131 - Electronics : Paper-I (Amplifiers)

P. Pages : 2

Time : Three Hours



GUG/S/17/3336

Max. Marks : 50

- Notes :
1. All questions are compulsory.
 2. All questions carry equal marks.
 3. Draw neat and labelled diagram wherever necessary.
 4. Use of log table / calculator is allowed.

1. Either

- a) What is amplifier ? Explain transistor as an amplifier. 5+
What is thermal runaway ? 5
Define :
i) Input resistance
ii) Output resistance
iii) Voltage gain

OR

- b) What are h-parameters? Explain them. 5+
Derive equations for h_{ie} and h_{re} in CE- Transistor amplifier. 5

2. Either

- a) Draw the ckt diagram of RC coupled amplifier and explain its working. 5+
What is distortion ? Explain frequency and phase distortion. 5

OR

- b) With circuit diagram explain the working of direct coupled amplifier. State advantages 5+
and disadvantages. 5
Explain Graphically class-A, class-B class-C and class-AB amplifier.

3. Either

- a) State the drawbacks of RC-coupled and direct coupled amplifiers. How are they 5+
overcome? 5
Draw the circuit diagram of differential amplifier and explain its working.

OR

- b) Draw the block diagram of operational amplifier and explain the function of each block ? 5+
Define : 5
i) Input bias current ii) Input off-set voltage
iii) Open loop gain iv) CMRR
v) Slew rate

4. **Either**
- a) Explain the working of op-Amp as a non inverting amplifier and derive an expression for its gain. **5+**
Explain op-Amp as an inverting adder. **5**

OR

- b) Explain op-Amp as an integrator. Prove that $V_0 = -\frac{1}{RC} \int V_{in} .dt$ **5+**
Explain the working of comparator using op-Amp. **5**
5. a) What is stability factor ? Explain its importance. **2½**
- b) Draw the frequency response curve of transformer coupled amplifier and explain. **2½**
- c) State the characteristics of ideal op-Amp. **2½**
- d) Explain the concept of virtual ground. **2½**
