



GUG/S/15/5603

B.Sc. (With Credits)-Regular-Semester 2012 Sem IV

**B.Sc.24132 Electronics-II**

**(Digital Electronics - II)**

**Paper - II**

P. Pages : 3

Time : Three Hours

Max. Marks : 50

- 
- Notes : 1. All questions are compulsory and carry equal marks.  
2. Draw neat diagrams wherever necessary.  
3. Use of log table / calculator is allowed.

**1.** Either

A) What is shift register? State its types. **3+7**

Draw block diagram of PIPO shift register.

Explain its construction and working.

**OR**

B) What is memory? Draw a block diagram **5+5** of MxN memory and explain.

Draw necessary diagram to obtain 4Kx8 memory using 1Kx8 memory chip.

Explain.

**2.** Either

- A) What is Read Only memory? Draw necessary diagram of 8x4 diode matrix ROM and explain.  
Draw and explain static Bipolar RAM cell.

**6+4**

**OR**

- B) Explain construction and working of charged couple device (CCD).

**5+5**

Explain the need and function of an on-chip decoding in a memory.

**3.** Either

- A) What is D/A converter? Define following parameters related to D/A converter.

**3+7**

i) Resolution ii) Linearity.

Draw circuit for 4-bit weighted type D/A converter and obtain formula for output voltage.

**OR**

- B) Explain working of 4-bit R-2R ladder type D/A converter with suitable diagram.

**7+3**

What will be the output voltage for such ladder for digital inputs:

i) 1010    ii) 1100    iii) full scale?

Given logic '0'=0V and logic '1'=10V.

4. Either

- A) Draw block diagram and explain function 10  
of each block of single slope A/D  
converter.

Draw necessary timing diagrams. State  
its draw backs.

OR

- B) Explain construction and working of 5+5  
successive approximation type A/D  
converter.

Explain the working of digital clock with  
suitable block diagram.

5. a) Give the classification of memory. 2½

- b) Explain the concept of flash memory. 2½

- c) State limitations of weighted register 2½  
ladder type D/A converter.

- d) Draw block diagram of digital frequency 2½  
meter.

\*\*\*\*\*