

S.Y.B.Sc.(Part-II)(With Credits)-Regular-Semester 2012 Sem IV
B.Sc.24132 - Electronics : Paper-II (Digital Electronics-II)

P. Pages : 1

GUG/S/17/5603

Time : Three Hours



Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat and well labelled diagram wherever necessary.
 3. Use of log table/ Calculator is allowed.

- 1. Either**
- a) What are left shift and right shift registers? 2+6+2
Explain the working of 4 bits right shift register and draw its necessary timing diagram. State any two applications of shift register.
- OR**
- b) Explain the expansion of memory size on the basis of 8+2
i) Word size, and
ii) Word capacity.
How many memory chips are required to design 2K bytes memory using 256 bytes of RAM chip.
- 2. Either**
- a) What are static and dynamic RAMs. 3+7
Explain construction and working of static RAM. Cell
- OR**
- b) Explain the basic structure of CCD. 3+5+2
Explain the operation of CCD.
State its any two applications.
- 3. Either**
- a) What are D/A and A/D converters? 2+2+6
Explain its need in digital systems.
Explain the working of weighted Resistor Ladder type D/A converter.
- OR**
- b) What are drawbacks associated with a weighted resistor ladder? 3+1+6
How are they removed in R-ZR ladder type D/A converter?
Explain working of R-2R ladder type D/A converter.
- 4. Either**
- a) Draw block diagram of digital clock. 3+7
Explain its principle and working.
- OR**
- b) Draw the block diagram of counter type A/D converter. 3+7
And explain its construction and working.
Draw its timing diagrams.
- 5.**
- a) What is buffer register? Explain. 2½ x 4
b) Draw diagram of MOS RAM Cell and explain its working.
c) What will be the output voltage of a 4 bit R-2R ladder for binary input of 1101.
Given logic 0 = 0V, Logic 1 = 8V
d) Explain the use and working of sample and hold circuit.
