



Electronics - II (Digital Electronics - II)
Paper - II

P. Pages : 3

Time : Three Hours

Max. Marks : 50

-
- Notes : 1. All questions are compulsory.
2. Each questions carry equal marks.
3. Draw neat diagram wherever necessary.
4. Use of log table/calculator is allowed.

1. Either

- a) Explain with the help of logic diagram, **5+5**
the working of the 4-bit SISO shift
register along with the timing diagram.
How are memories classified on the
basis of media, speed and data storage
capacity.

OR

- b) Explain the working and importance of **5+5**
controlled 4-bit buffer register,
A RAM chip of 256 byte capacity is
available. How many chips are needed
to obtain a memory of 2K bytes?
Draw its necessary diagram

2. Either

- a) Explain the construction and working of bipolar RAM cell. **5+5**
Explain the operation of charge coupled device (CCD)

OR

- b) Explain construction and working of diode matrix ROM. **5+5**
Explain the need and function of an on-chip decoding in a memory.

3. Either

- a) Explain the working of a 4-bit weighted resistor type D/A converter. **6+2+2**
State its drawbacks.
How can it be improved by using op-amp.

OR

- b) Explain the working of 4-bit R – 2R ladder type D/A converter with suitable diagram. **6+4**
What will be the output voltage of 4-bit R – 2R ladder corresponding to the binary inputs i) 1010 ii) 0101, where logic '0' = 0V and logic '1' = 8V?

4. a) State the principle and explain the working of a single slope A/D converter. **6+4**
Explain the working of successive approximation A/D converter with suitable diagram.

OR

- b) Draw the block diagram of dual slope type ADC. **2+5+3**
Explain its working alongwith timing diagram.
Give the advantages and disadvantages of dual slope A/D converter.
5. a) Explain with the help of logic diagram, the working of the 4-bit shift left register. **2.5**
- b) Explain difference between static and dynamic RAM cell. **2.5**
- c) Explain the need of ADC and DAC in electronic instrumentation system. **2.5**
- d) Draw the block diagram of digital clock. **2.5**
