

S.Y.B.Sc.(Part-II)(With Credits)-Regular-Semester 2012 Sem IV
B.Sc.24132 - Electronics-II (Digital Electronics-II) Paper-II

P. Pages : 2

Time : Three Hours



GUG/W/17/5603

Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat diagrams wherever necessary.
 3. Use of log table / calculator is allowed.

1. Either

- a) What is shift register ? 1+
What is the necessity of shift register ? 3+
Draw the diagram of 4-bit SISO shift register and explain its construction and working. 6

OR

- b) What is memory ? Give the classification of semiconductor memories. 6+
Obtain 8 kbyte memory using 1 kbyte. 4
Draw suitable diagram.

2. Either

- a) What is Read only memory ? Draw necessary diagram of 8 x 4 diode matrix ROM and explain its working. Explain the need and function of an on-chip decoding in a memory. 5+
5

OR

- b) Explain the MOS RAM. State its advantages. 5+
Explain the construction and working of charge couple device (CCD). 5

3. Either

- a) Explain the following D/A converter parameter - 6+
i) Range 4
ii) Resolution
iii) Linearity
In 4-bit weighted D/A converter, find the analog output for digital input 1011, 0111 and 1111. (Given logic '1' = +8V and logic '0' = 0V)

OR

- b) Draw the circuit diagram of 4 bit R-2R ladder D/A converter and explain its working 10
Derive the expression for its output voltage. State its advantages.

4. Either

- a) Explain the construction and working of counter type analog to digital converter with timing diagram. 6+
Explain the following A/D converter parameter : 4
i) Resolution ii) Speed

OR

- b) Draw the block diagram of a single slope A/D converter and give importance of each block in brief. **10**
State the drawbacks associated with a single slope A/D converter.
5. a) Explain the working of 4-bit controlled buffer register. **2½**
- b) Differentiate between static and dynamic RAM. **2½**
- c) State the disadvantages of weighted type D/A converter. **2½**
- d) Draw the block diagram of digital clock. **2½**
